

Write the hardware description of a 8-bit register with shift left and shift right modes of operation and test its operation.